

# Signal Processing Electronics

---

B.Satyanarayana

Tata Institute of Fundamental Research, Mumbai

Contact: [bsn@tifr.res.in](mailto:bsn@tifr.res.in)

# Plan of the course

- Lecture – 1
  - ❖ Basic concepts, from signals to DAQ systems
- Lecture – 2
  - ❖ Signal transmission, preamplifiers, shaping amplifiers, discriminators, coincidence circuits and instrumentation standards
- Lecture – 3
  - ❖ Analog-to-Digital, Time-to-Digital Converters and modern DAQ system elements
- Examples from CMS, ALICE and INO experiments

# Part-III

Monday, July 4, 2011

---

**Acknowledgements & References:** G.Hall, W.R.Leo, Jörgen Christiansen, GRAPES collaboration , Ortec, P.Horowitz & W.Hill, C.F.G.Delaney



# Analogue to Digital Conversion

- Turns electrical input (voltage/current) into numeric value
- Parameters and requirements
  - ❖ Resolution
    - the granularity of the digital values
  - ❖ Integral Non-Linearity
    - proportionality of output to input
  - ❖ Differential Non-Linearity
    - uniformity of digitisation increments
  - ❖ Conversion time
    - how much time to convert signal to digital value
  - ❖ Count-rate performance
    - how quickly a new conversion can begin after a previous event
  - ❖ Stability
    - how much values change with time

# Analog-to-Digital Converters (ADCs)



- Peak-sensing
  - ❖ Maximum of the voltage signal is digitised
  - ❖ Ex: Signal of the PMT in voltage mode (slow signals, already integrated)
- Charge sensitive
  - ❖ Total integrated current digitised
  - ❖ Ex: Signal of the PMT in the current mode (fast signals)
- Time of integration or the time period over which the ADC seeks a maximum is determined by the width of the gate signal

# Types of ADCs

- Ramp or Wilkinson
- Successive approximation
- Flash or parallel
- Sigma-delta ADC
- Hybrid (Wilkinson + successive approximation)
- Tracking ADC
- Parallel ripple ADC
- Variable threshold flash ADC
- ...



# Ramp or Wilkinson ADC

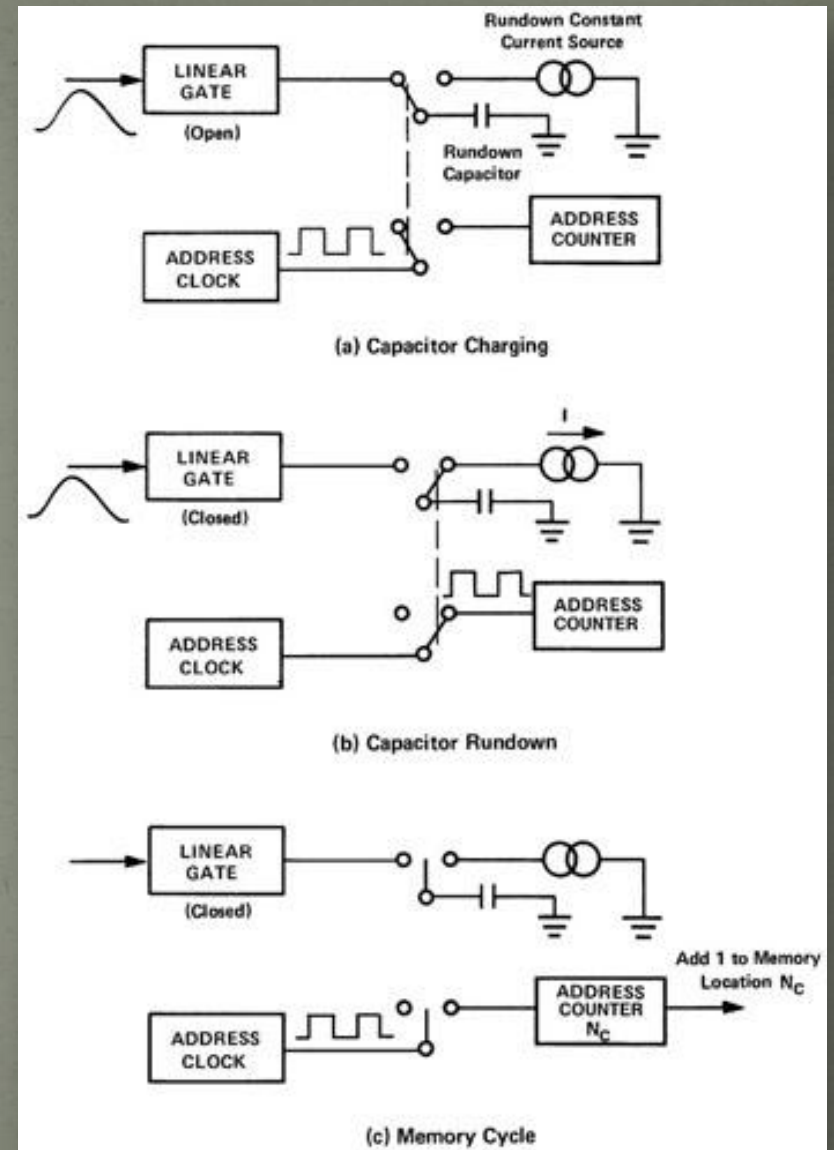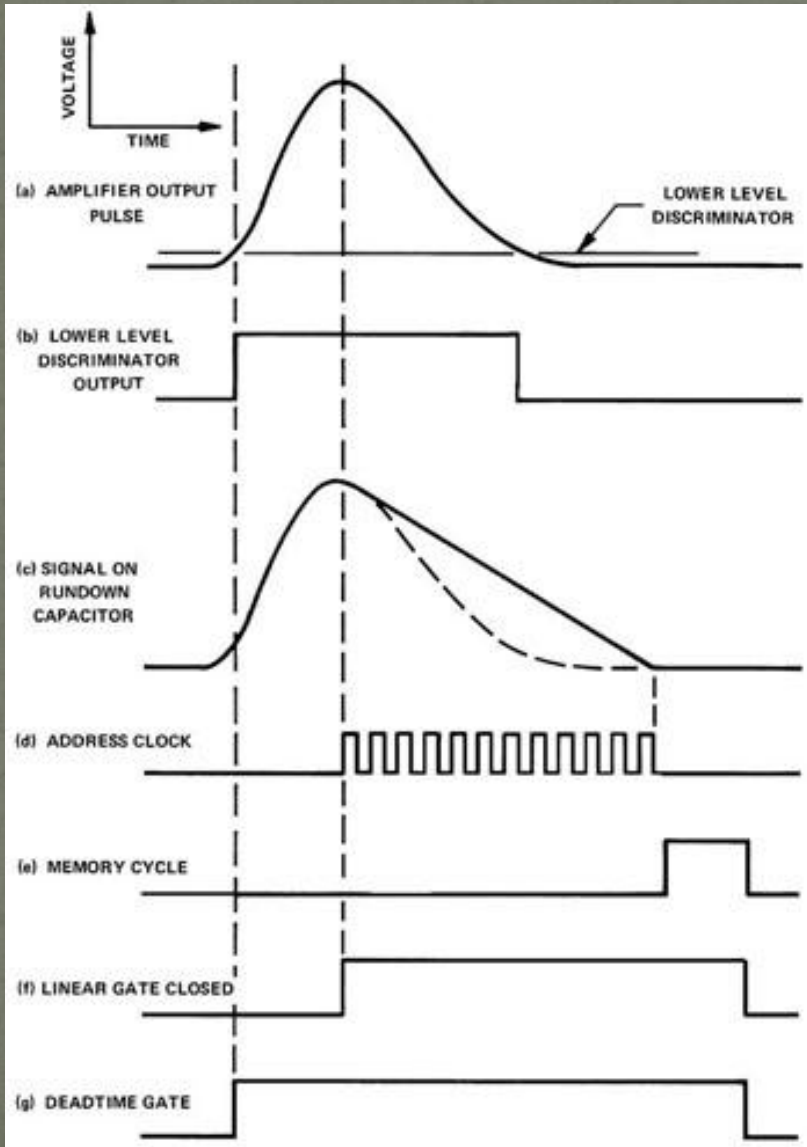

# Successive approximation ADC

- analogous to binary search


generate  $V_{ref} = \Delta V \times (2^{N-1}, 2^{N-2}, \dots 2^0)$  in N steps

set bit = 1

if  $V_{in} > V_{ref}$

leave

else bit = 0

 

- Pros


speed  $\sim \mu\text{sec}$

high resolution

- Cons

DNL 10-20%

 *very precise resistors required with DAC for  $V_{ref}$*




DAC = digital to analogue converter  
ie number  $\rightarrow$  voltage


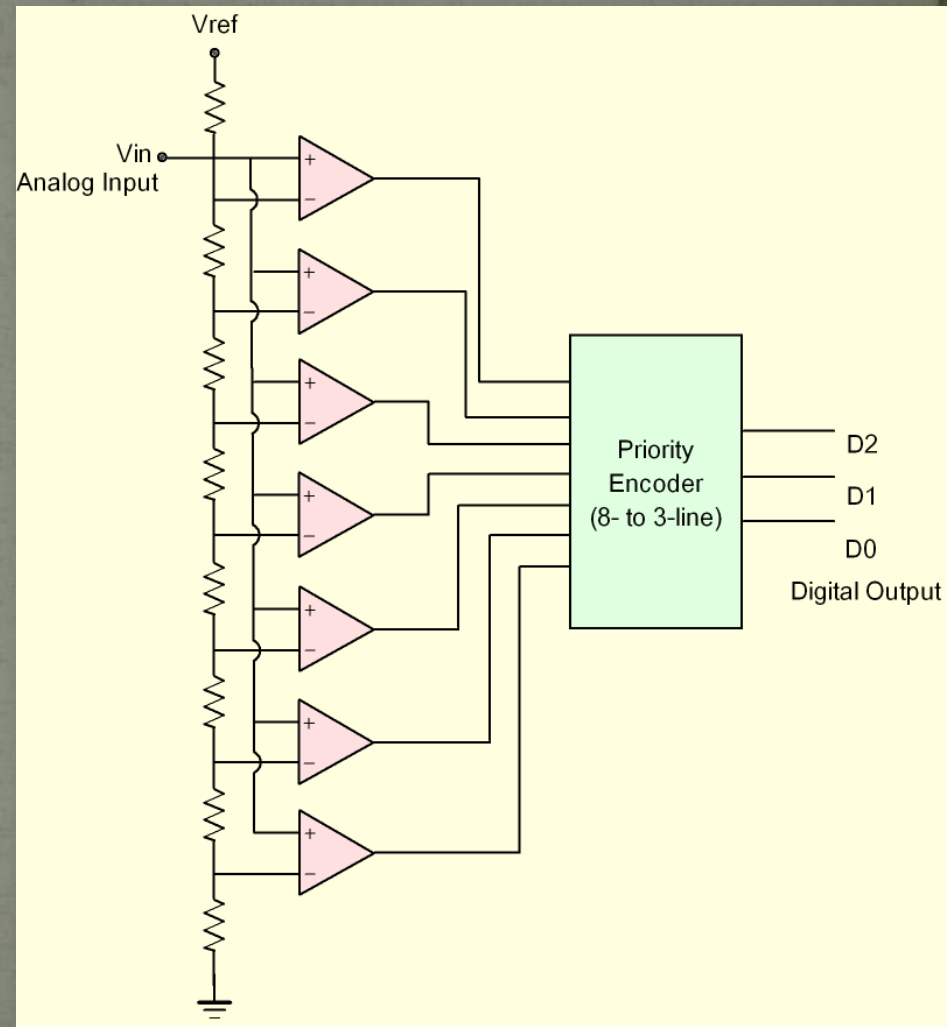
# Flash or parallel ADC

- Flash ADC is the fastest ADC type available. The digital equivalent of the analog signal will be available right away at its output – hence the name “flash”.
- The number of required comparators is  $2^n - 1$ , where  $n$  is the number of output bits.
- Since Flash ADC comparisons are set by a set of resistors, one could set different values for the resistors in order to obtain a non-linear output, i.e. one value would represent a different voltage step from the other values.



# Sigma-delta ADC

- Digitise the signal with 1-bit resolution at a high sampling rate (MHz).  
useful for high resolution conversion of low-frequency signals, to 20bits  
low-distortion conversion of audio signals  
good linearity and high accuracy.

- Operation - At  $t = 0$ , assume  $V_{ref} = 0$

$V_{out}$  high

integrator charges -ve

at rate  $\sim V_{in}$

comparator flips

counter goes low


clock increments... etc,...

$V_{in} = 0 \Rightarrow$  output = 000000...

$V_{in} = (1/2)V_{in}(\max) \Rightarrow$  output = 101010...

$V_{in} = V_{in}(\max) \Rightarrow$  output = 111111...


 
the higher the input voltage, the more 1's at the serial digital output.


  
# Integral non-linearity

- Output value  $D$  should be linearly proportional to  $V$
- Check with plot

- For more precise evaluation of INL fit to line and plot deviations
- Plot  $D_i - D_{fit}$  vs  $nchan$





# Differential non-linearity

- Measures non-uniformity in channel profiles over range

$$DNL = DV_i / \langle DV \rangle - 1$$



$DV_i$  = width of channel  $i$

$\langle DV \rangle$  = average width

- RMS or worst case values may be quoted

DNL  $\sim$  1% typical but  $10^{-3}$  can be achieved

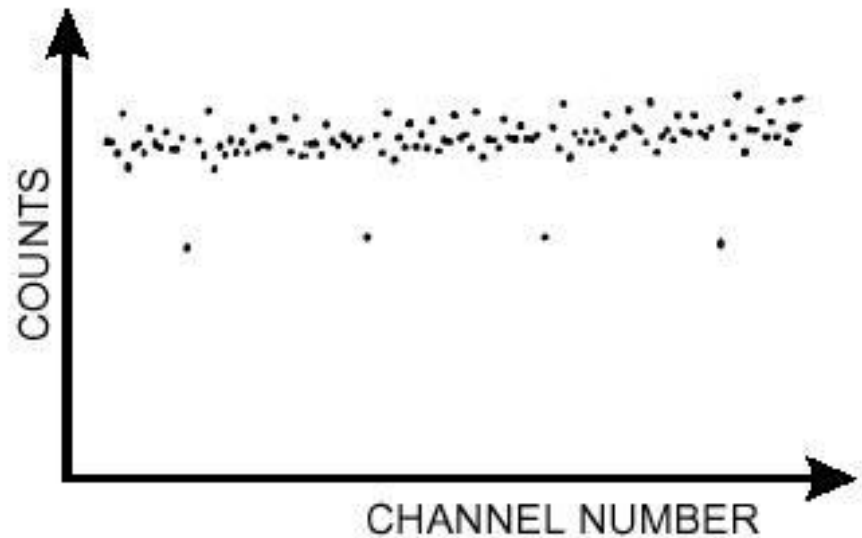 can show up systematic effects, as well as random



# Resolution


- To convert an analogue value, eg voltage, to digital two parameters are required range and number of bits

$$\text{quantum} = \Delta V = (V_{\max} - V_{\min}) * 2^{-N} \quad \text{referred to as 1LSB (least significant bit)}$$

- eg 10 bits =  $2^{10} = 1024$ ,  $V_{\max} - V_{\min} = 1V \Rightarrow \Delta V = 1V/1024 \approx 1mV$

- Ideal ADC behaviour

probability vs amplitude

 


- Real ADC behaviour

noise in digitisation process

smears resolution

$$\sigma_{\text{noise}} < \Delta V/4$$

 

# Other variables

- Conversion time
  - ❖ finite time is required for conversion and storage of values
  - ❖ may depend on signal amplitude
  - ❖ gives rise to dead time in system
  - ❖ i.e. system cannot handle another event during dead time
  - ❖ may need accounting for, or risk bias in results
- Rate effects
  - ❖ results may depend on rate of arrival of signals
  - ❖ typically lead to spectral broadening
- Stability
  - ❖ temperature effects are a typical cause of variations
- A partial solution to most of these problems is regular calibration, preferably under real operating conditions, as well as control of variables



# Non-linear ADC

- A integrating system for measuring x-ray photons for crystallography, measuring spots. The most intense spots contain up to  $\sim 10^9$  photons, the weakest just a few.

Measure  $N$  in spot

aim: achieve 1% resolution

using a 10-bit ADC (cost)

assume 1V range

1V = largest signal, defines  $G_1$

$N < 10^4$   $\sigma(N)/N > 1\%$

defines smallest signals


but ADC LSB  $>$  signal

Increase small signal gain  $G_2$

Select output in ADC range

- Is 1% resolution achieved for all  $N$ ?

If not... ?

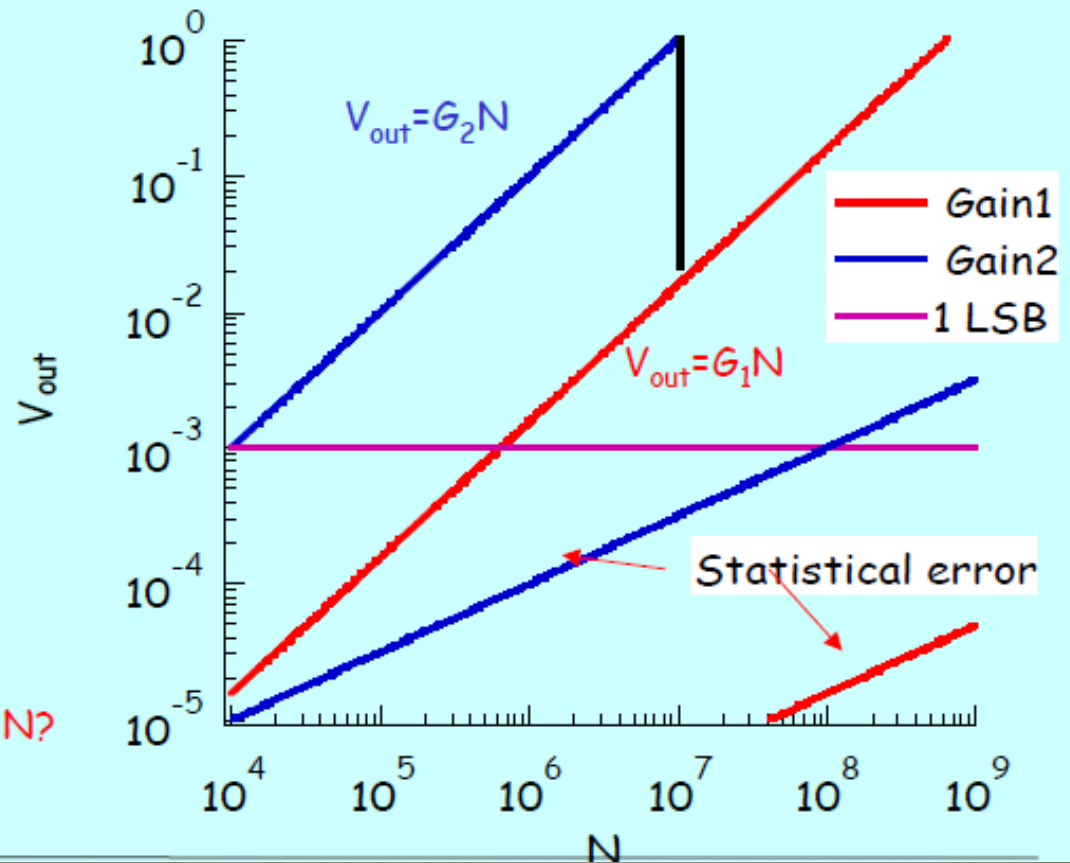


# Why TDCs?

TDCs are used to measure time or intervals

 
## ❖ Start – Stop measurement

- Measurement of time interval between two events:  
Start signal – Stop signal
- Used to measure relatively short time intervals with high precision
- Like a stop watch used to measure sport competitions


 
## ❖ Time tagging

- Measure time of occurrence of events with a given time reference:  
Time reference (Clock)  
Events to be measured (Hits)
- Used to measure relative occurrence of many events on a defined time scale:  
Such a time scale will have limited range; like 12/24 hour time scale on your watch when having no date and year



# Where TDCs?

- Special needs for High Energy Physics
  - ❖ Many thousands of channels needed
  - ❖ Rate of measurements can be very high
  - ❖ Very high timing resolution
  - ❖ A mechanism to store measurements during a given interval and extract only those related to an interesting event, signaled by a trigger, must be integrated with TDC function
- Other applications
  - ❖ Laser/radar ranging to measure distance between cars
  - ❖ Time delay reflection to measure location of broken fiber
  - ❖ Most other applications only needs one or a few channels



# How to compare TDCs?

- Merits
  - ❖ Resolution
    - Bin size and effective resolution (RMS, INL, DNL)
  - ❖ Dynamic range
  - ❖ Stability
    - Use of external reference
    - Drift (e.g. temperature)
    - Jitter and Noise
  - ❖ Integration issues
    - Digital / analog
    - Noise / power supply sensitivity
    - Sensitivity to matching of active elements
    - Required IC area
    - Common timing block per channel
    - Time critical block must be implemented on chip together with noisy digital logic
- Use in final system
  - Can one actually use effectively very high time resolution in large systems (detectors)
  - Calibration - stability
  - Distribution of timing reference (start signal or reference clock)
  - Other features: data buffering, triggering, readout, test, radiation, etc.

# Basic TDC types - I



- Counter type

- ❖ Advantages

- Simple; but still useful!
- Digital
- large dynamic range possible
- Easy to integrate many channels per chip

- ❖ Disadvantages

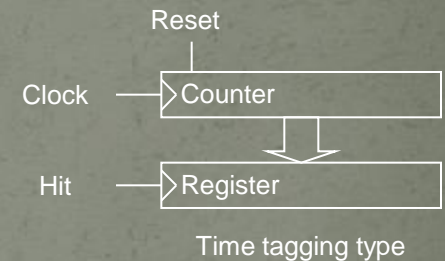 - Limited time resolution (1ns using modern CMOS technology)
- Meta stability (use of Gray code counter)





- Single Delay chain type

- ❖ Cable delay chain (distributed L-C)

- Very good resolution (5ps/mm)
- Not easy to integrate on integrated circuits


- ❖ Simple delay chain using active gates

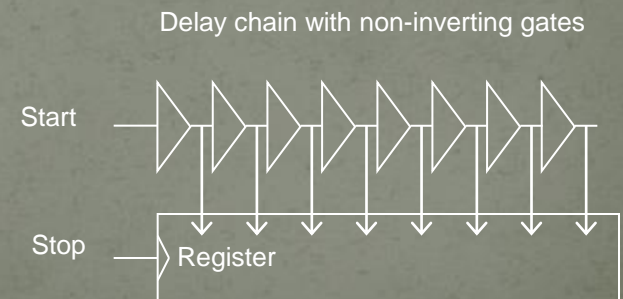 - Good resolution (~100ps using modern tech)
- Limited dynamic range (long delay chain and register)
- Only start-stop type
- Large delay variations between chips and with temperature and supply voltage





# Counter-type TDC

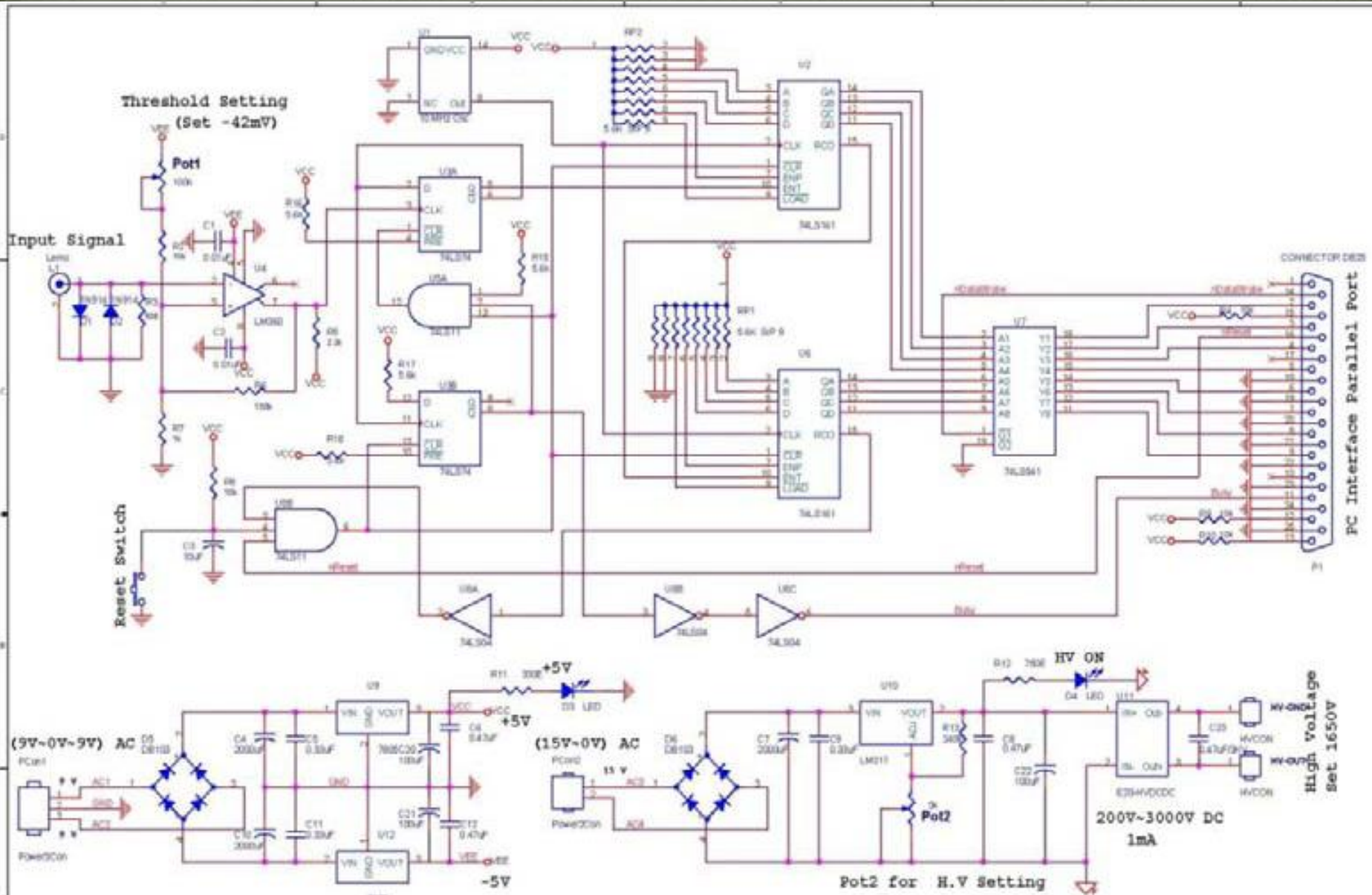




# Basic TDC types - II

- Single Delay chain type (Contd ...)


- ❖ Delay locked loop

 - Self calibrating using external frequency reference (clock)
- Allows combination with counter
- Delicate feedback loop design (jitter)



- ❖ R-C delay chain

 - Very good resolution
- Signal slew rate deteriorates
- Delay chain with losses; so only short delay chain possible
- Large sensitivity to process parameters (and temperature)




# Basic TDC types - III

- Multiple delay chain type


- ❖ Vernier delay chain types

 - Resolution determined by delay difference between two chains. Delay difference can be made very small and very high resolution can be obtained.
- Small dynamic range (long chains)
- Delay chains can not be directly calibrated using DLL
- Matching between delay cells becomes critical



- ❖ Coupled delay locked loops

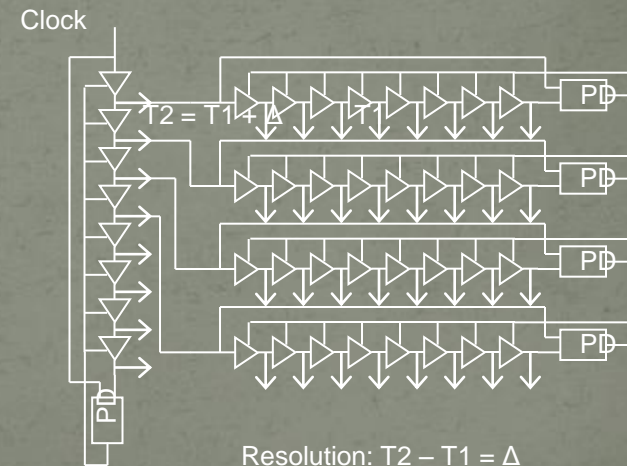- Sub-delay cell resolution ( $1/4$ )
- All DLLs use common time reference (clock)
- Common timing generator for multiple channels
- Jitter analysis not trivial



# Basic TDC types - IV

- Charge integration

- ❖ Using ADC (TAC)




- High resolution
- Low dynamic range
- Sensitive analog design
- Low hit rate
- Requires ADC

- ❖ Using double slope (time stretcher)

- No need for ADC (substituted with a counter)



- Multiple *exotic* architectures

   - ❖ Heavily coupled phase locked loops
- ❖ Beating between two PLLs
- ❖ Re-circulating delay loops
- ❖ Summing of signals with different slew rates






# Time-to-Amplitude Converter (TAC)

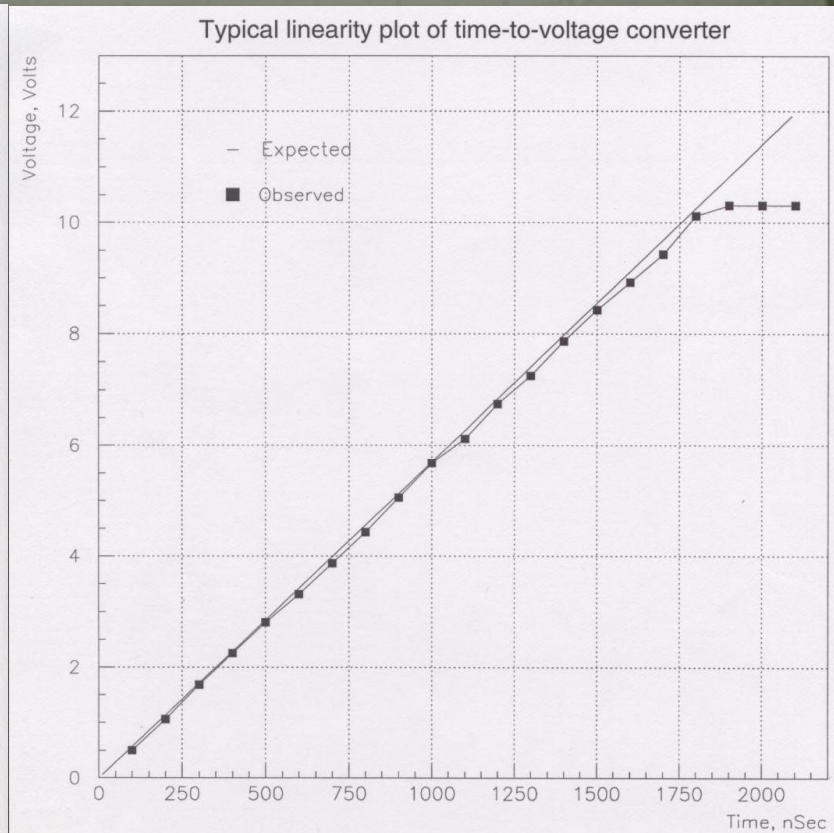
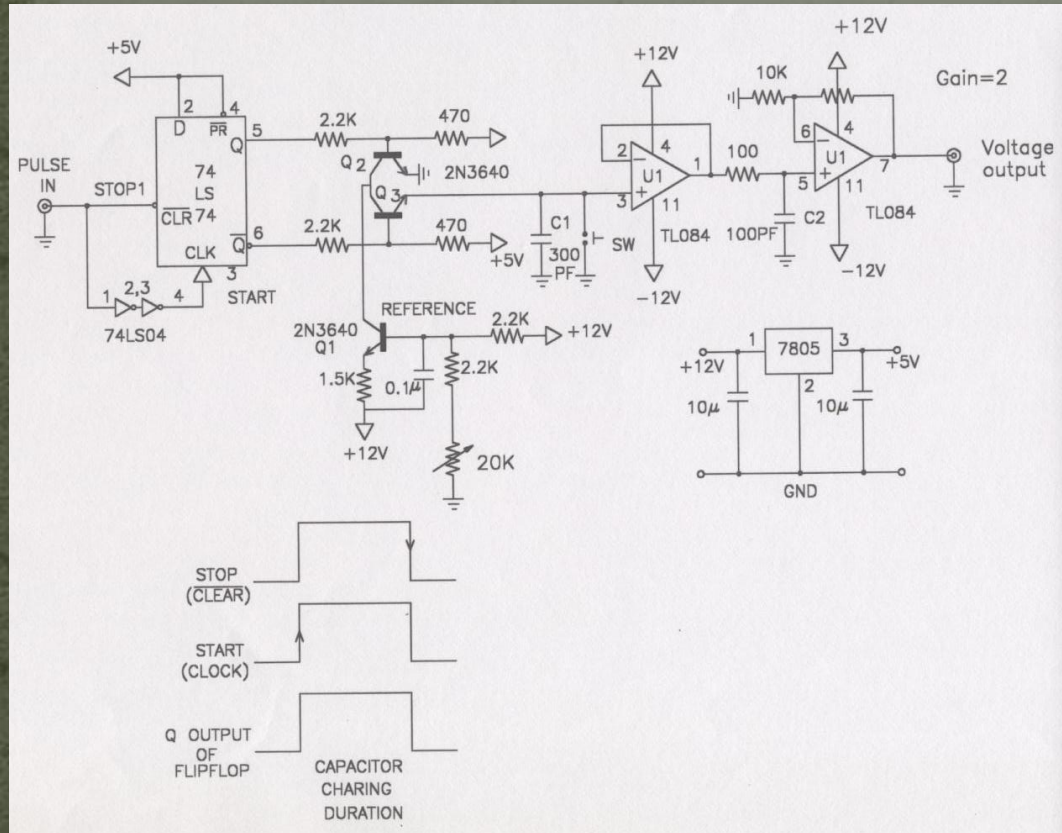


# Architecture of HPTDC (ALICE TOF)

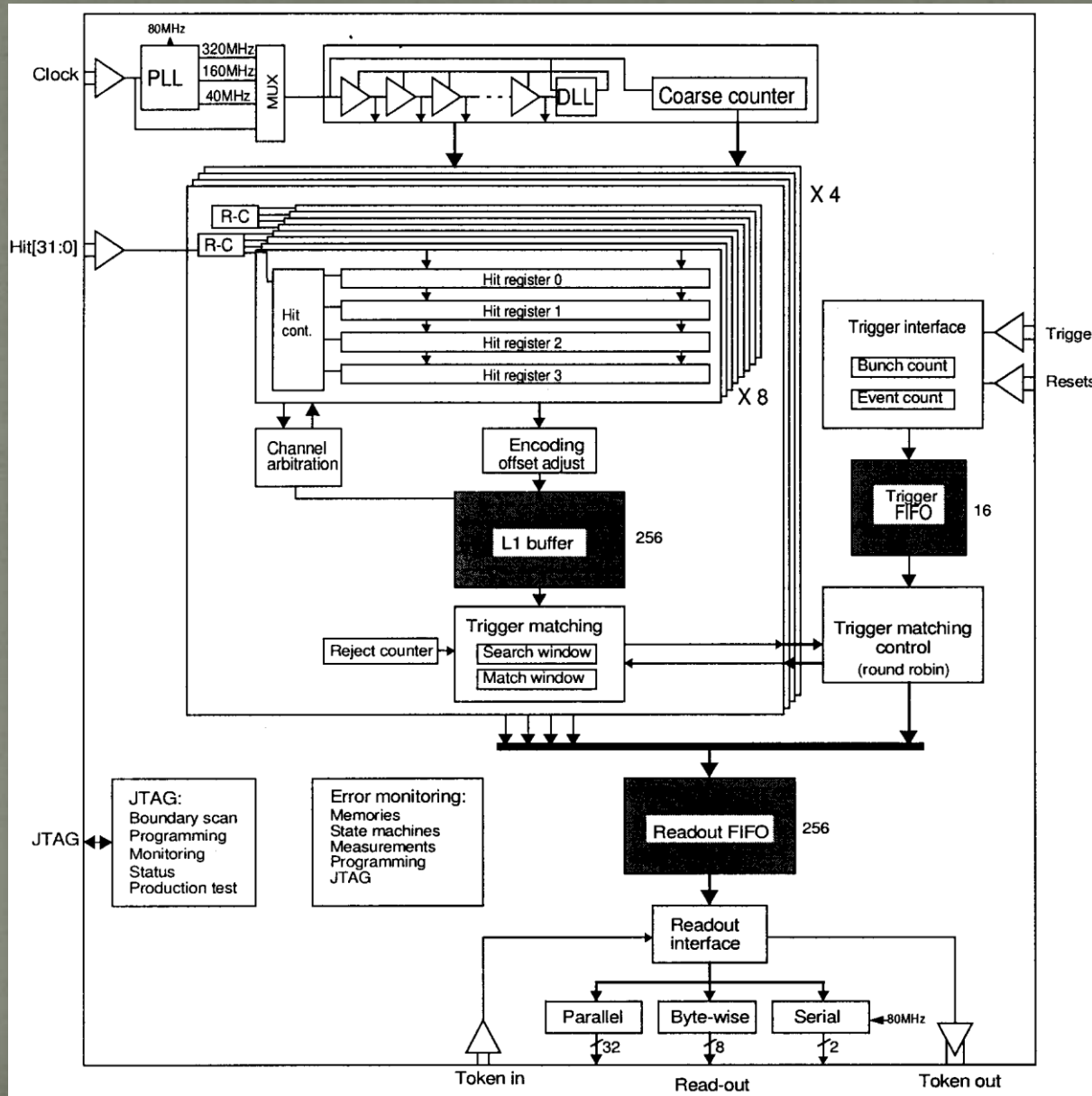
 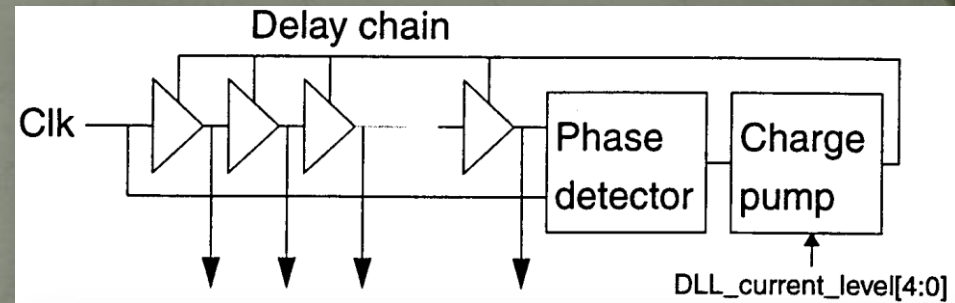
# Delay Locked Loop (DLL)


- Three major components:
  - Chain of 32 delay elements; adjustable delay
  - Phase detector between clock and delayed signal
  - Charge pump & level shifter generating control voltage to the delay elements
- Jitter in the delay chain
- Lock monitoring
- Dynamics of the control loop
- Programmable charge pump current level





 
# Coarse time count

- Dynamic range of the fine time measurement, extracted from the state of DLL is expanded, by
- Storing the state of a clock synchronous counter
- Hit signal is synchronous to the clocking, so
- Two count values,  $\frac{1}{2}$  a clock cycle out of phase stored
- At reset, coarse time counter loaded with time offset



 


# HPTDC's DNL and INL


- Differential Non-Linearity(DNL) is defined as the variation of any code from an ideal 1 LSB step.
- $DNL(n) = (Actual(n)/Expected(n)) - 1$ .
- Integral Non-Linearity (INL) is the deviation of the transfer function from a reference line measured in fractions of 1 LSB using a best straight line. INL is simply the integral of the DNL.
- So if we can get the DNL then we can compute the INL.
- In HPTDC the base clock is 40 MHz i.e. 25ns so the DNL pattern repeats every 25ns.



# HPTDC's DNL test result

 

# HPTDC's INL test result

 

# HPTDC's DNL/INL data correction

- The fixed pattern in the INL is caused by 40 MHz cross talk from the logic part of the chip to the time measurement part .
- As this crosstalk comes from the 40MHz clock, which is also the time reference of the TDC, the integral non linearity have a stable shape between chips and can therefore be compensated for using the LSB bits of the measurements.


Test Condition	Effective resolution (RMS)
<b>98ps resolution</b>	<b>64ps</b>
<b>98ps resolution after INL correction</b>	<b>34ps</b>
<b>24ps resolution</b>	<b>58ps</b>
<b>24ps resolution after INL correction</b>	<b>17ps</b>



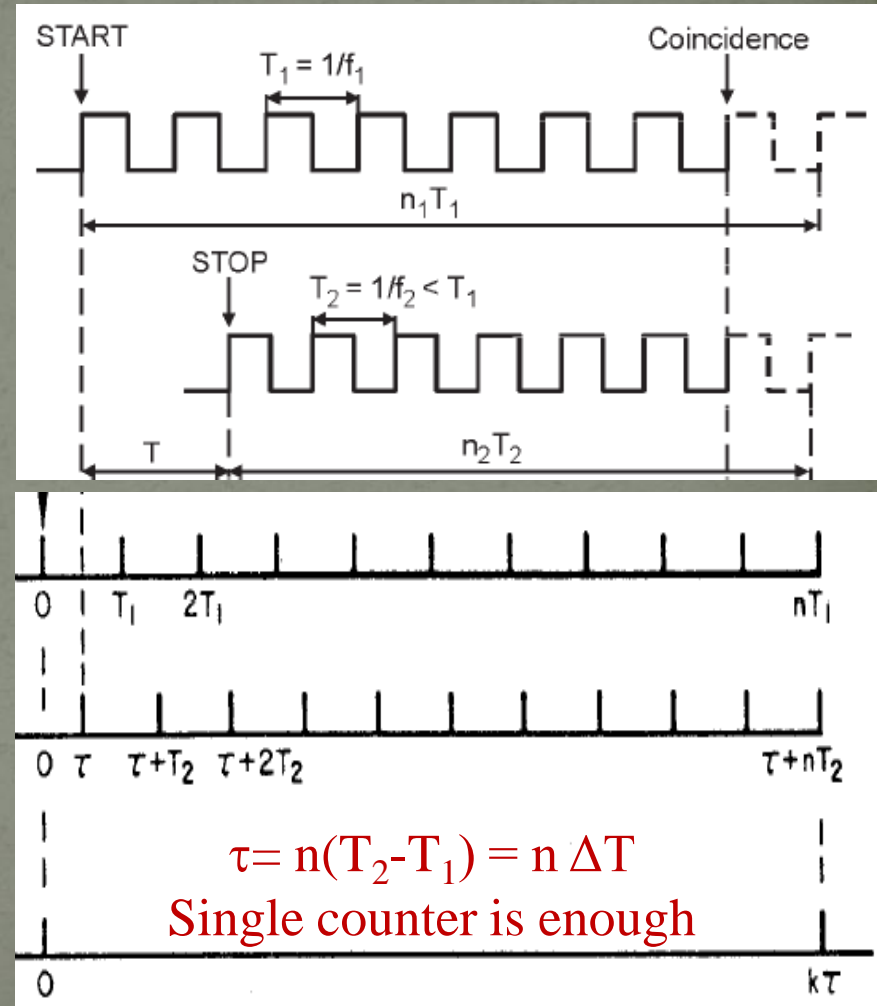
# Concept of vernier TDC

- Two clocks of slightly different periods  $T_1$  and  $T_2$  ( $T_1 > T_2$ ) are employed.
- START pulse will start the slow oscillator ( $T_1$ ) and STOP pulse will start the fast oscillator ( $T_2$ ).
- Since  $T_2 < T_1$ , fast oscillator will catch up with the slow one.
- The time interval between the START and STOP can be measured as:  


$$T = (N_1 - 1) T_1 - (N_2 - 1) T_2$$
- Two counters for  $N_1$  and  $N_2$  needed.



# Schematic of vernier TDC

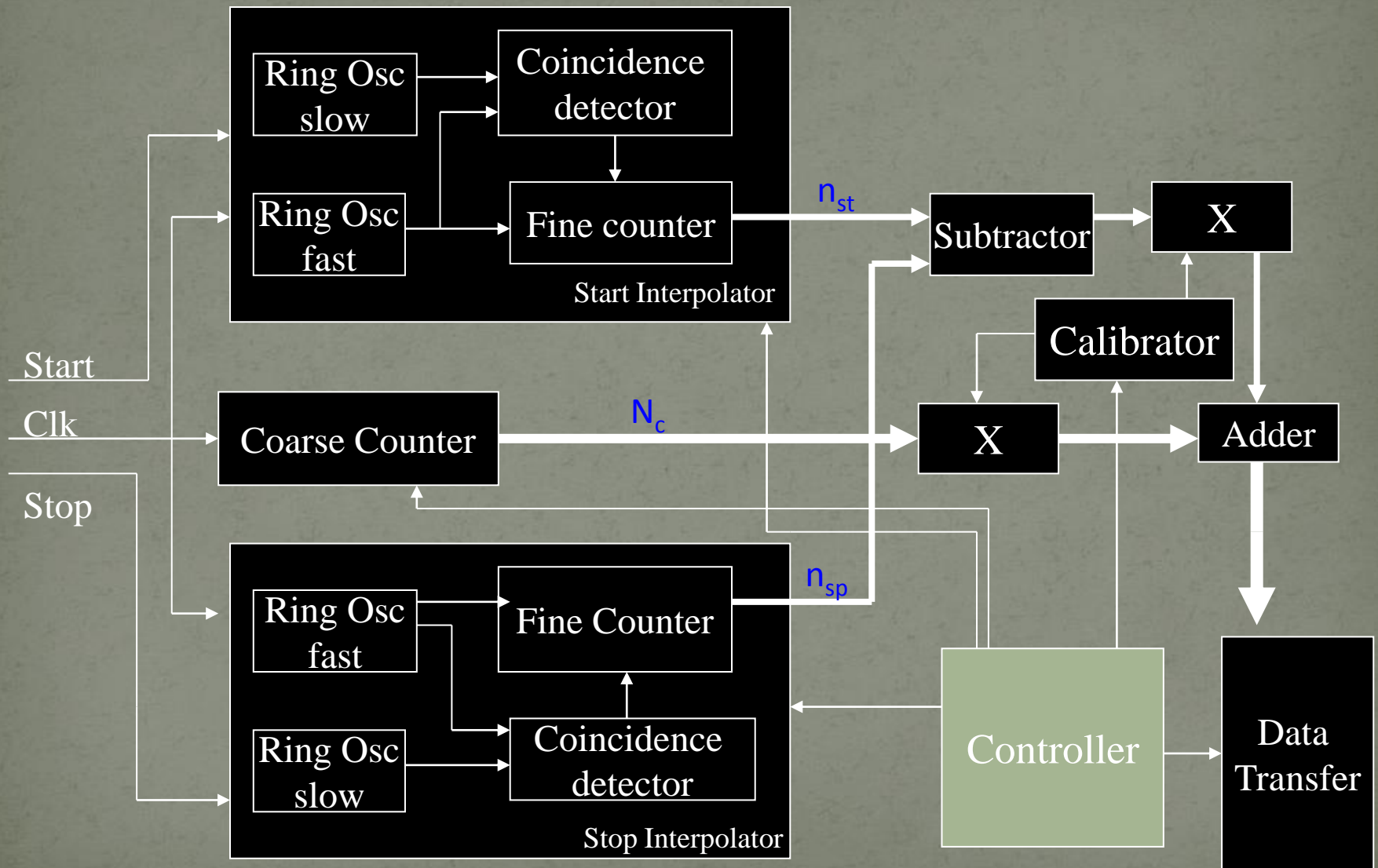


# Switched Capacitor Array

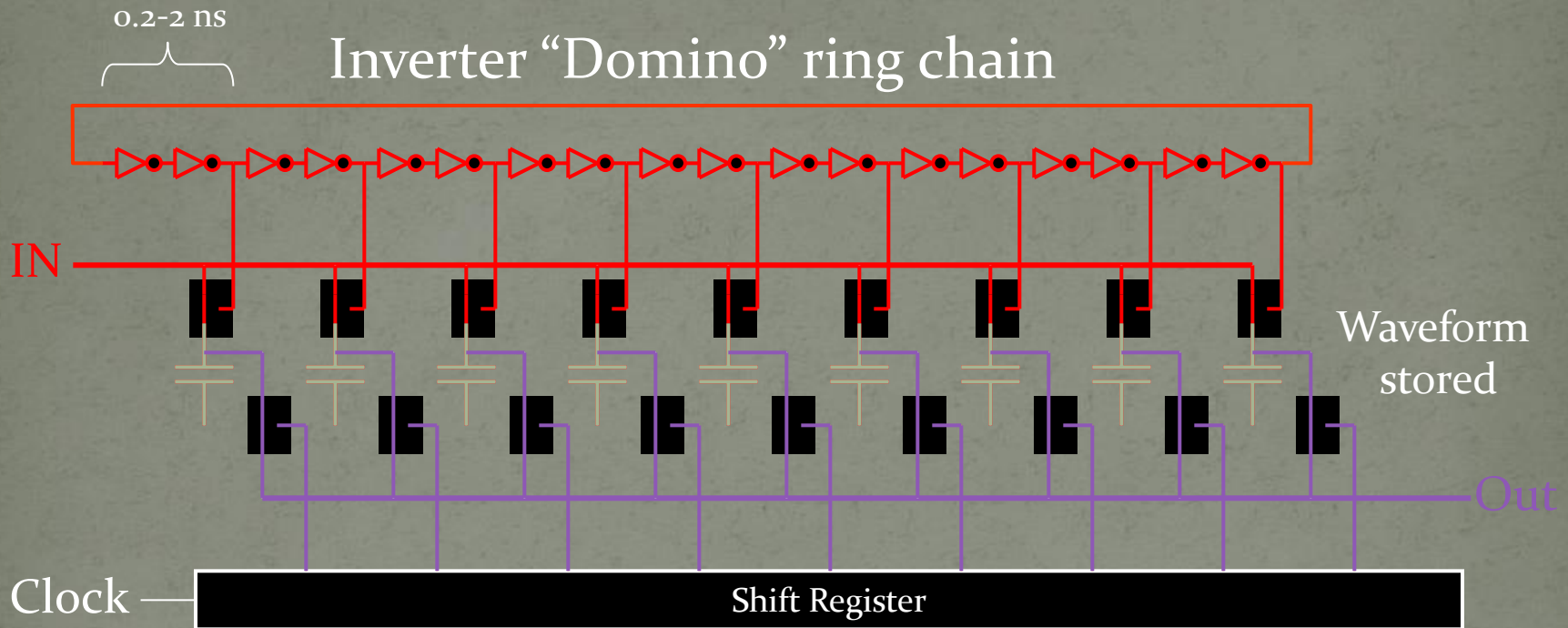


"Time stretcher" GHz  $\rightarrow$  MHz



# Functional block diagram of DRS4

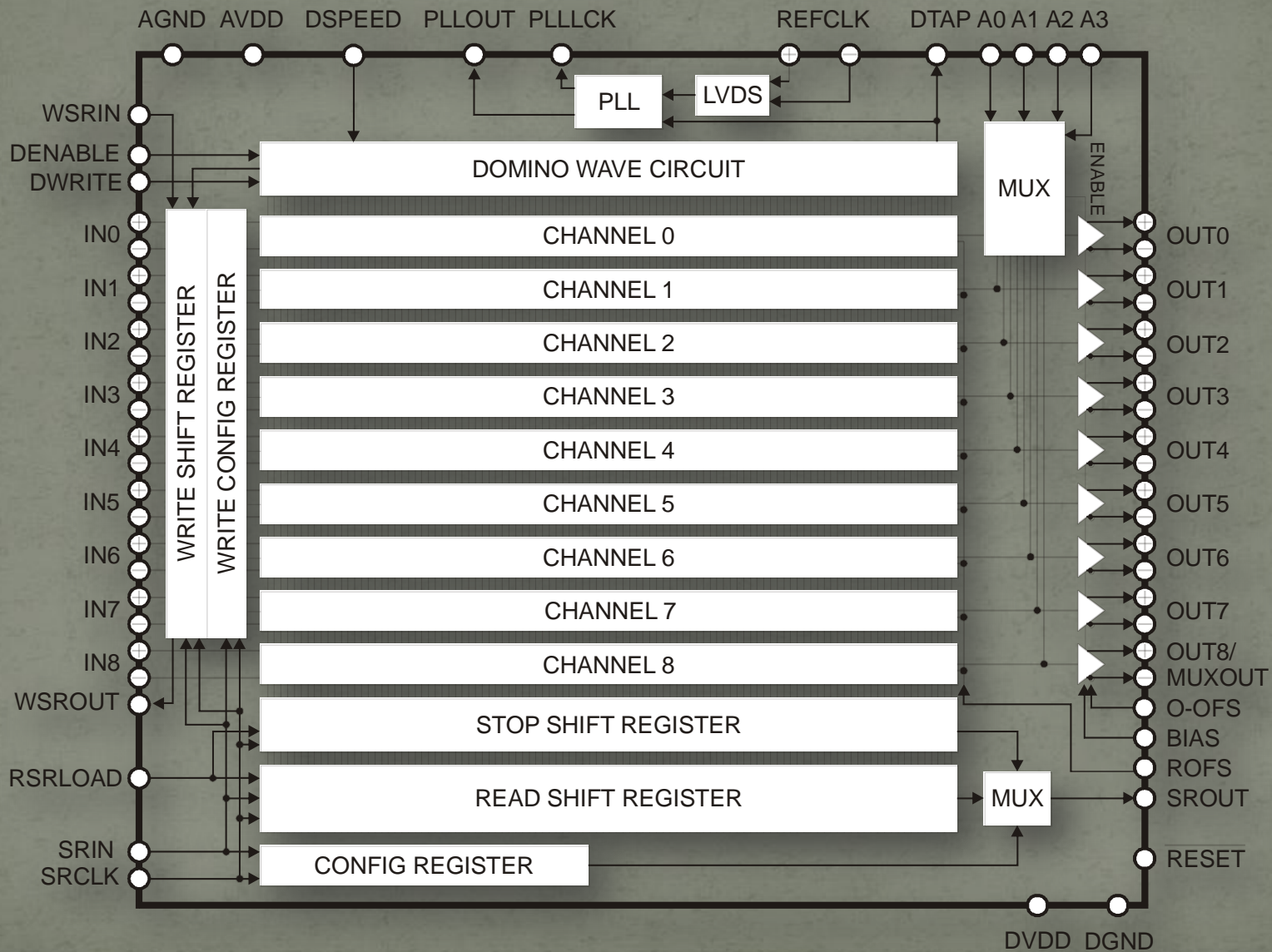

# Data acquisition through DRS chip

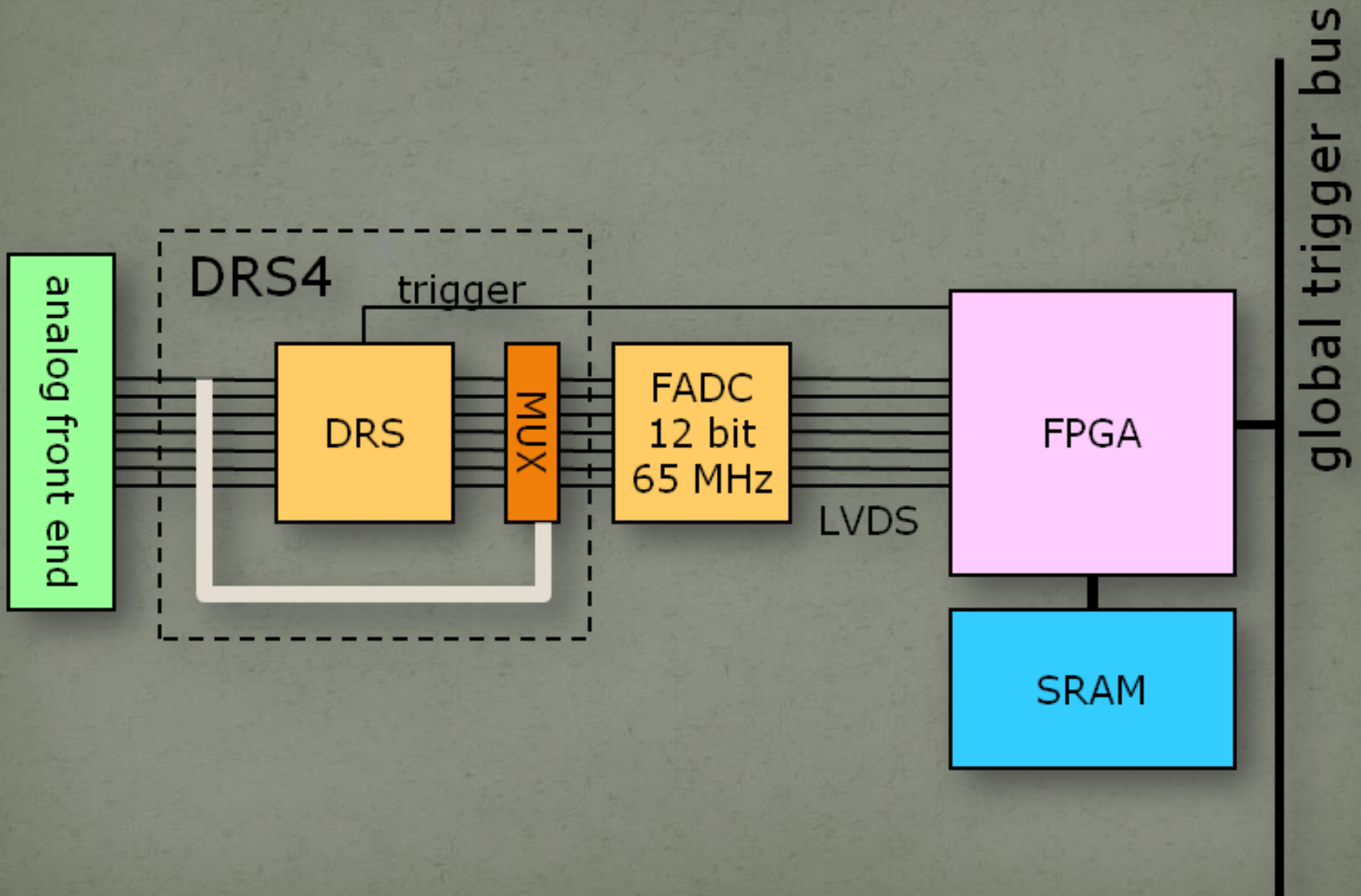

# Thank you

---

For your attention.